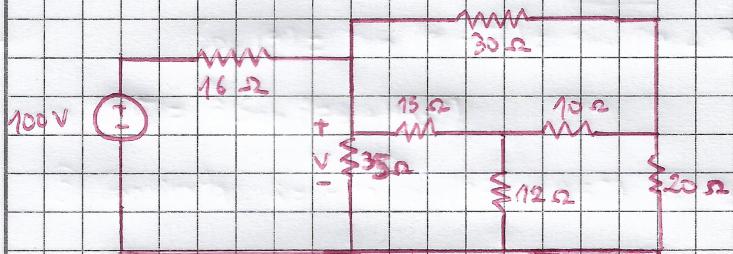



Ejercicio 2.56 Fundamentos de Circuitos - Charles K. Andrew.

2.56 Determine V en el circuito de la figura 2.120.



$$R_a = \frac{(15)(10) + (12)(10) + (15)(12)}{12}$$

$$R_a = 37.5 \Omega$$

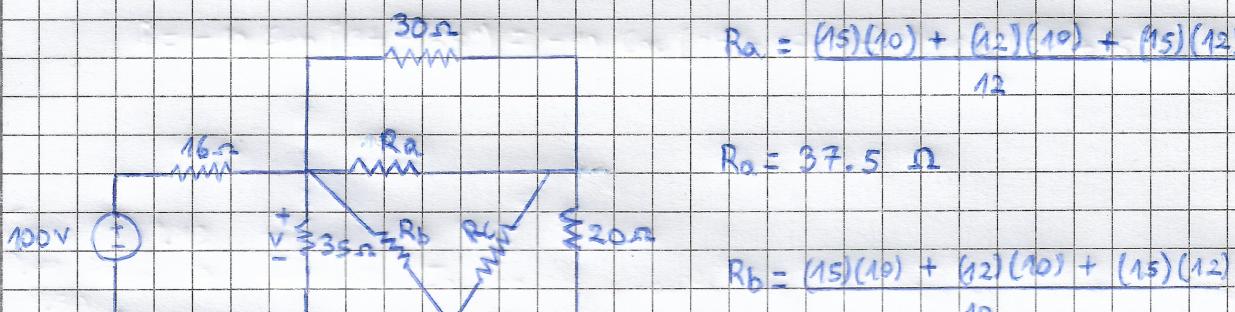

$$R_b = \frac{(15)(10) + (12)(10) + (15)(12)}{10}$$

$$R_b = 45 \Omega$$


$$R_c = \frac{(15)(10) + (15)(12) + (10)(12)}{15}$$

$$R_c = 30 \Omega$$

$$R_{eq_1} = \frac{(35)(45)}{35 + 45} = \frac{315}{16} \Omega$$


$$R_{eq_2} = \frac{(30)(20)}{30 + 20} = 12 \Omega$$
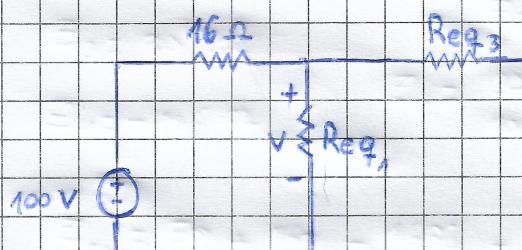
$$R_{eq_3} = \frac{(37.5)(30)}{37.5 + 30} = \frac{50}{3} \Omega$$



$$Req_4 = Req_3 + Req_2 = \frac{86}{3} \Omega$$
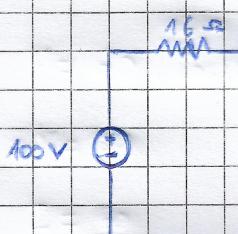
$$Req_5 = \frac{Req_4 \cdot Req_1}{Req_4 + Req_1} = 11.7$$



$$Req = 16 + 11.7 = 27.7 \Omega$$

$$I = \frac{100}{27.7} = 3.61 [A]$$

$$V = (11.7)(3.61) = 42.24 [V]$$